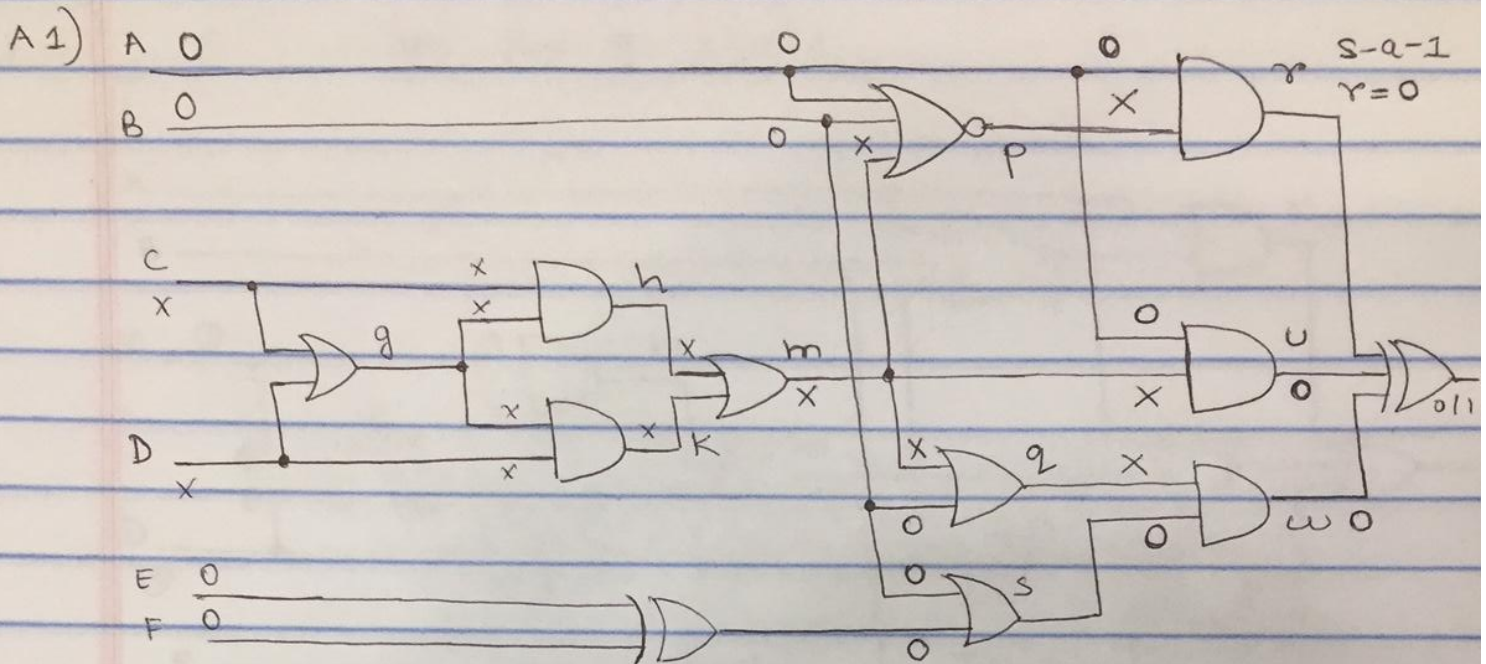


Homework K-5




Test for the fault r s-a-1


- For r stuck at 1, we initially take $r=0$
- In order to allow r to change and output change be detected both u and w is made as 0 and following the circuit path the input vector is arrived at.
- There are two possibilities of input vectors for the circuit above which are 00xx00 or 00xx11 since for the last E&F inputs to the XOR gate need to be either both 0 ($E=0$ and $F=0$) or 1 ($E=1$ and $F=1$).

1 b)

Test for g s-a-1

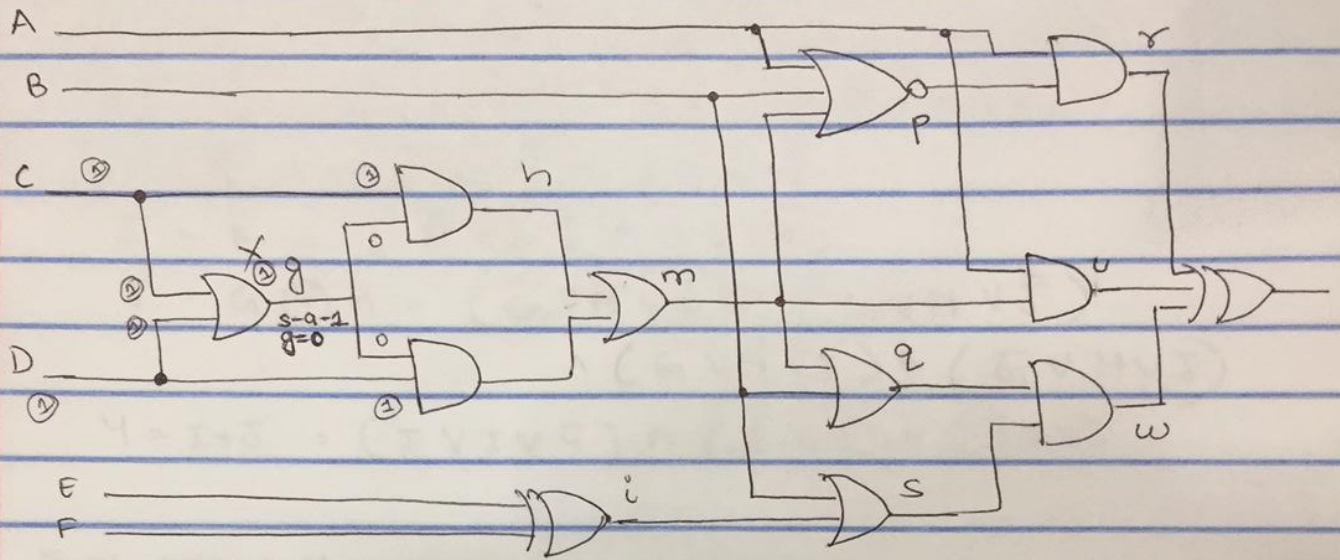

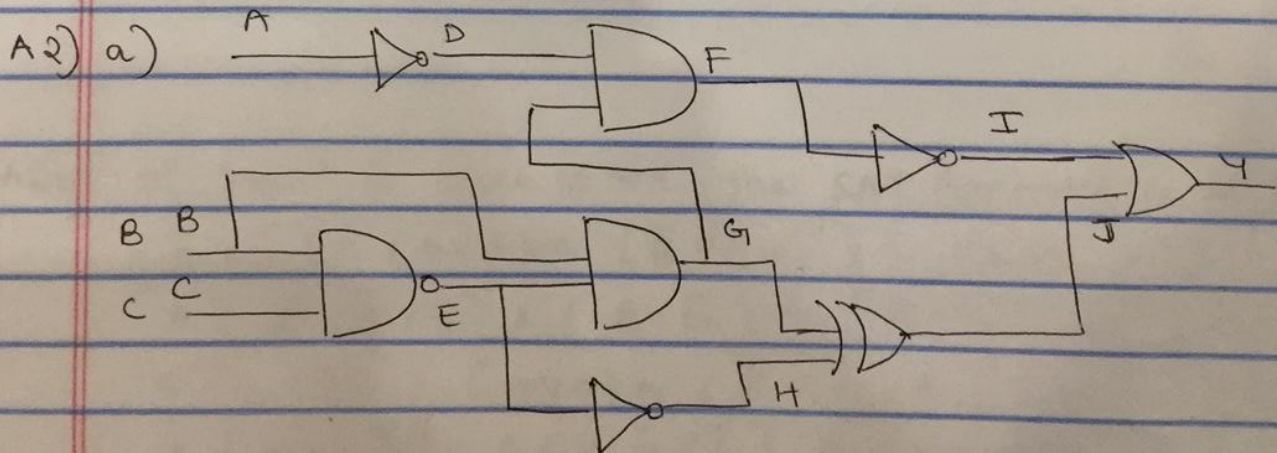As shown in above figure when g s-a-1, we put $g=0$ in order to propagate through the circuit and we see that there is no such input vector.



Applying Tseitin Transformation :-

$$D = \bar{A} = (\bar{A} \vee \bar{D}) \wedge (A \vee D)$$

$$E = \bar{B} \cdot C = (\bar{B} \vee \bar{C} \vee \bar{E}) \wedge (B \vee E) \wedge (C \vee E)$$

$$G = BE = (\bar{B} \vee \bar{E} \vee G) \wedge (B \vee \bar{G}) \wedge (E \vee \bar{G})$$

$$F = DG = (\bar{D} \vee \bar{G} \vee F) \wedge (D \vee \bar{F}) \wedge (G \vee \bar{F})$$

$$H = \bar{E} = (\bar{E} \vee \bar{H}) \wedge (E \vee H)$$

$$I = \bar{F} = (\bar{F} \vee \bar{I}) \wedge (F \vee I)$$

$$J = G \oplus H = (\bar{G} \vee \bar{H} \vee \bar{J}) \wedge (G \vee H \vee \bar{J}) \\ \wedge (G \vee \bar{H} \vee J) \wedge (\bar{G} \vee H \vee J)$$

$$Y = I + J = (I \vee J \vee \bar{Y}) \wedge (\bar{I} \vee Y) \wedge (\bar{J} \vee Y)$$

∴ Final output Y =

$$(\bar{A} \vee \bar{D}) \wedge (A \vee D) \wedge (\bar{B} \vee \bar{C} \vee \bar{E}) \wedge (B \vee E) \wedge (C \vee E) \wedge (\bar{B} \vee \bar{E} \vee G) \\ \wedge (B \vee \bar{G}) \wedge (E \vee \bar{G}) \wedge (\bar{D} \vee \bar{G} \vee F) \wedge (D \vee \bar{F}) \wedge (G \vee \bar{F}) \\ \wedge (\bar{E} \vee \bar{H}) \wedge (E \vee H) \wedge (\bar{F} \vee \bar{I}) \wedge (F \vee I) \wedge (\bar{G} \vee \bar{H} \vee \bar{J}) \\ \wedge (G \vee H \vee \bar{J}) \wedge (G \vee \bar{H} \vee J) \wedge (\bar{G} \vee H \vee J) \wedge (I \vee J \vee \bar{Y}) \\ \wedge (\bar{I} \vee Y) \wedge (\bar{J} \vee Y) \wedge Y$$

A26) If net F is stuck at one. The SAT formula is as follows:-

$$(\bar{A} \vee \bar{D}) \wedge (A \vee D) \wedge (\bar{B} \vee \bar{C} \vee \bar{E}) \wedge (B \vee E) \wedge (C \vee E) \\ \wedge (\bar{B} \vee \bar{E} \vee G) \wedge (B \vee \bar{G}) \wedge (E \vee \bar{G}) \wedge (\bar{D} \vee \bar{G} \vee 1)^1 \\ \wedge (D \vee 0) \wedge (G \vee 0) \wedge (\bar{E} \vee \bar{H}) \wedge (E \vee H) \wedge (0 \vee \bar{I}) \\ \wedge (1 \vee \bar{I})^1 \wedge (\bar{G} \vee \bar{H} \vee \bar{J}) \wedge (G \vee H \vee \bar{J}) \wedge (G \vee \bar{H} \vee J) \\ \wedge (\bar{G} \vee H \vee J) \wedge (I \vee J \vee \bar{Y}) \wedge (\bar{I} \vee Y) \wedge (\bar{J} \vee Y) \wedge Y$$

$$\begin{aligned} \text{AQC)} \quad & (\bar{A} \vee \bar{D}) \wedge (A \vee D) \wedge (\bar{B} \vee \bar{C} \vee \bar{E}) \wedge (B \vee E) \wedge (C \vee E) \\ & \wedge (\bar{B} \vee \bar{E} \vee G) \wedge (B \vee \bar{G}) \wedge (E \vee \bar{G}) \wedge (\bar{D} \vee G \vee F) \\ & \wedge (D \vee \bar{F}) \wedge (G \vee \bar{F}) \wedge (\bar{E} \vee \bar{H}) \wedge (E \vee H) \wedge (\bar{F} \vee \bar{I}) \\ & \wedge (F \vee I) \wedge (\bar{G} \vee \bar{H} \vee \bar{J}) \wedge (G \vee H \vee \bar{J}) \wedge (G \vee \bar{H} \vee J) \\ & \wedge (\bar{G} \vee H \vee J) \wedge (I \vee J \vee \bar{Y}) \wedge (\bar{I} \vee Y) \wedge (\bar{J} \vee Y) \\ & \wedge Y \wedge \bar{J} \wedge \bar{F} \end{aligned}$$

Since the ~~one~~ F is stuck at 1, we put \overline{F} as and to the SAT formula, also using path sensitization \overline{J} has to be made 0 \therefore , \overline{J} is added to the SAT formula.

	A	B	C	D	E	F	G	H	I	J	K
	1	2	3	4	5	6	7	8	9	10	11
$\bar{A}V\bar{D}$	-1	-4	0								
$A\bar{V}D$	1	4	0								
$\bar{B}V\bar{C}V\bar{E}$	-2	-3	-5	0							
$B\bar{V}E$	+2	+5	0								
$C\bar{V}E$	3	5	0								
$\bar{B}V\bar{E}V\bar{G}$	-2	-5	7	0							
$B\bar{V}\bar{G}$	2	-7	0								
$E\bar{V}\bar{G}$	5	-7	0								
$\bar{D}V\bar{G}V\bar{F}$	-4	-7	6	0							
$D\bar{V}\bar{F}$	4	-6	0								
$G\bar{V}\bar{F}$	7	-6	0								
$\bar{E}V\bar{H}$	-5	-8	0								
$E\bar{V}H$	5	8	0								
$\bar{F}V\bar{I}$	-6	-9	0								
$F\bar{V}I$	6	9	0								
$\bar{G}V\bar{H}V\bar{J}$	-7	-8	-10	0							
$G\bar{V}H\bar{V}\bar{J}$	7	8	-10	0							
$G\bar{V}\bar{H}V\bar{J}$	7	-8	10	0							
$\bar{G}VH\bar{V}\bar{J}$	-7	8	10	0							
$\bar{I}V\bar{J}V\bar{K}$	9	10	-11	0							
$\bar{I}V\bar{K}$	-9	11	0								
$\bar{J}V\bar{K}$	-10	11	0								
K											
\bar{K}											
F											

$ABC = 000$
 $put A = 1$
 $ABC = 100$

$ABC = 000$
 put $A = 1$
 $ABC = 100$
 if we force $B = 1 \Rightarrow$ unsat
 if we force $C = 1$

$$ABC = \underline{001}$$

If we force $A=1, C=1$

$$ABC = \underline{101}$$

Ans